

Assessment Assignment 1
 Course CSE350
 Section 05
 Faculty [ZAZ] Ihzaz Abrar Sadik
 Semester Spring 2026



Total Marks 20
 Bonus Marks 3
 Start 27 February 2026
 Deadline **14 March 2026**
 Obtained Marks out of **20**

ID:		Name:	
------------	--	--------------	--

Q1:

Let an analog signal have values in the range $[-4(n+1)+2, 4(n+1)+2]$. Where, 'n' is the last digit of your student ID. This signal is converted to a $(\text{mod}((n+1), 2) + 2)$ -bit digital signal using the fastest ADC available. This digital signal is then passed to a DAC of the same number of bits. The DAC has doubled resistances at its input branches.

- What type of ADC & DAC were used? What is the bit number? [4]
- Make a table listing the quantization intervals & the corresponding outputs from the DAC. [6]
- If the input to the ADC is 'n+1', find the output at the DAC end. [3]
- If you take $R = R_F$ for the DAC, find its reference voltage(s). [6]
- If another signal $(n+1) + (n+1) \sin(\omega t)$ of frequency $\frac{n+1}{4} \text{ kHz}$ is passed as the input to the same ADC-DAC combination, and sampling is done at a rate of $(n+1) \text{ kHz}$, find the output from the DAC for the first 3 samples. [4]